

EX 1: MANUAL CALCULATION OF Y-BUS MATRIX

GIVEN DATA

Line 1 : Bus 1 – Bus 2

$$Z_{12} = 0.10 + j0.40 \text{ p.u.}$$

$$\text{Line Charging Admittance} = j0.015 \text{ p.u.}$$

Line 2 : Bus 2 – Bus 3

$$Z_{23} = 0.15 + j0.60 \text{ p.u.}$$

$$\text{Line Charging Admittance} = j0.020 \text{ p.u.}$$

Line 3 : Bus 3 – Bus 4

$$Z_{34} = 0.18 + j0.55 \text{ p.u.}$$

$$\text{Line Charging Admittance} = j0.018 \text{ p.u.}$$

Line 4 : Bus 4 – Bus 1

$$Z_{41} = 0.10 + j0.35 \text{ p.u.}$$

$$\text{Line Charging Admittance} = j0.012 \text{ p.u.}$$

Line 5 : Bus 4 – Bus 2

$$Z_{42} = 0.25 + j0.20 \text{ p.u.}$$

$$\text{Line Charging Admittance} = j0.030 \text{ p.u.}$$

SOLUTION:

STEP 1: CALCULATION OF LINE ADMITTANCES

$$Y_{12} = 1/(0.10 + j0.40) = (0.10 - j0.40)/(0.10^2 + 0.40^2) = -0.5882 - j2.3529 \text{ p.u.}$$

$$Y_{23} = 1/(0.15 + j0.60) = (0.15 - j0.60)/(0.15^2 + 0.60^2) = -2.3922 + j1.5666 \text{ p.u.}$$

$$Y_{34} = 1/(0.18 + j0.55) = (0.18 - j0.55)/(0.18^2 + 0.55^2) = -0.5378 - j1.6420 \text{ p.u.}$$

$$Y_{41} = 1/(0.10 + j0.35) = (0.10 - j0.35)/(0.10^2 + 0.35^2) = -0.7547 + j2.6415 \text{ p.u.}$$

$$Y_{42} = 1/(0.25 + j0.20) = (0.25 - j0.20)/(0.25^2 + 0.20^2) = -2.4390 + j0.9512 \text{ p.u.}$$

STEP 2 : OFF-DIAGONAL ELEMENTS

$$Y_{12} = Y_{21} = -0.5882 + j2.3529$$

$$Y_{23} = Y_{32} = -2.3922 + j1.5666$$

$$Y_{34} = Y_{43} = -0.5378 + j1.6420$$

$$Y_{13} = Y_{31} = -0.5882 + j2.3529$$

$$Y_{24} = Y_{42} = 0$$

STEP 3 : DIAGONAL ELEMENTS

$$Y_{11} = Y_{12} + Y_{14} + (j0.015/2) + (j0.012/2)$$

$$= (0.5882 - j2.3529) + (0.7547 - j2.6415) + j0.0075 + j0.006 = 1.3429 - j4.9809$$

$$Y_{22} = Y_{12} + Y_{23} + Y_{24} + (j0.015/2) + (j0.020/2) + (j0.030/2)$$

$$= (0.5882 - j2.3529) + (0.3922 - j1.5686) + (2.4390 - j1.9512) + j0.0325 = 3.4194 - j6.8602$$

$$Y_{33} = Y_{23} + Y_{34} + (j0.020/2) + (j0.018/2)$$

$$= (0.3922 - j1.5686) + (0.5378 - j1.6420) + j0.019 = 0.9980 - j3.1960$$

$$Y_{44} = Y_{14} + Y_{24} + Y_{34} + (j0.012/2) + (j0.018/2) + (j0.030/2)$$

$$= (0.7547 - j2.6415) + (2.4390 - j1.9512) + (0.5378 - j1.6420) + j0.030 = 3.7313 - j6.7070$$

FINAL Y-BUS MATRIX

$$\begin{bmatrix} 1.3429 - j4.9809 & -0.5882 + j2.3529 & -0.5882 + j2.3529 & 0 \\ -0.5882 + j2.3529 & 3.4194 - j6.8602 & -2.3922 + j1.5666 & -0.7547 + j2.9412 \\ 0 & -0.3922 + j1.5866 & 0.9980 - j3.1960 & -0.5378 + j1.6420 \\ -0.7547 + j2.6415 & -2.4390 + j1.9512 & -0.5378 + j1.6420 & 3.7313 - j6.7070 \end{bmatrix}$$